



# Combinational Logic

*Rab Nawaz Khan Jadoon*

Lecturer

**COMSATS Lahore**

**Pakistan**

Department of Computer Science

**DCS**

COMSATS Institute of  
Information Technology

**Digital Logic and Computer Design**

# COMBINATIONAL LOGIC

Introduction

Design Procedure

Adders

Half Adder

Full Adder

Parallel Adder

Subtractors

Half Subtractor

Full Subtractor


Code Conversion

# Combinational logic

- A **combinational circuit** consists of logic gates whose outputs at any time are determined directly from the present combination of inputs without regard to previous outputs.
- A **combinational circuit** performs a specific information processing operation fully specified logically by a set of Boolean functions.
- A **Combinational circuit** consists of input variables, logic gates, and output variables.
 
# Combinational logic

- The logic gate accepts signals from the inputs and generates signals to the outputs.
- This process transforms binary information from the given input data to the required output data.



# Combinational logic

## ■ Design Procedures

- Starts from the verbal outline of the problem and ends in a logic circuit diagram.
- The procedure involves the following step,
  - The problem is stated.
  - Input and required output variables are determined.
  - Assigned the variables letter symbols.
  - Make the truth table.
  - The simplified Boolean functions for each output is obtained.
  - The logic diagram is drawn.

# Combinational logic

## ■ Adders

- Adders are important in computers and also in other types of digital systems in which numerical data are processed.
- An understanding of the basic adder operation is fundamental to the study of digital systems.
- The most basic operation is no doubt is the addition of two binary digits.



# The Half Adder

## ■ Half Adder

- The combinational circuit that performs the additions of two bit is called Half adder.
- One that performs the addition of three bits including two digits and one previous carry is a full adder.
- Two half adders can be employed to form a full adder.



## ■ Half Adder

- It has two inputs and two outputs.
- The input variables designates the augends and addend bits; the output variables produces the sum and carry.
- It is necessary to specify two output variables because the result may consist of two binary digits.
- A and B are two inputs binary variables while C and S used for carry and Sum to the outputs.




# Combinational logic
 
## ■ Half Adder

- The half-adder accepts two binary digits on its inputs and produces two binary digits on its outputs, a sum bit and a carry bit.
- The truth table look like this,

$0 + 0 = 0$
$0 + 1 = 1$
$1 + 0 = 1$
$1 + 1 = 10$




<b>A</b>	<b>B</b>	<b>C<sub>out</sub></b>	<b>S</b>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

# Combinational logic
 
## ■ Half Adder

- A half-adder is represented by the logic symbol in Figure below,



## ■ Half-Adder Logic

- Notice that the output Carry ( $C_{out}$ ) is a 1 only when both A and B are 1s; therefore  $C_{out}$  can be expressed as the AND of the input variables.
- $C_{out} = AB$
- Now observe that the sum output ( $\Sigma$ ) is a 1 only if the input variables, A and B, are not equal.
- The sum can therefore be expressed as the exclusive-OR of the input variables.

$$\Sigma = A \oplus B$$

# Related Example


## ■ Half-Adder Logic

- The logic implementation required for the half adder function can be developed.
- The output carry is produced with an AND gate with A and B on the inputs.
- The sum output is generated with an exclusive-OR gate.







# Half Adder

- Half-Adder Logic diagram

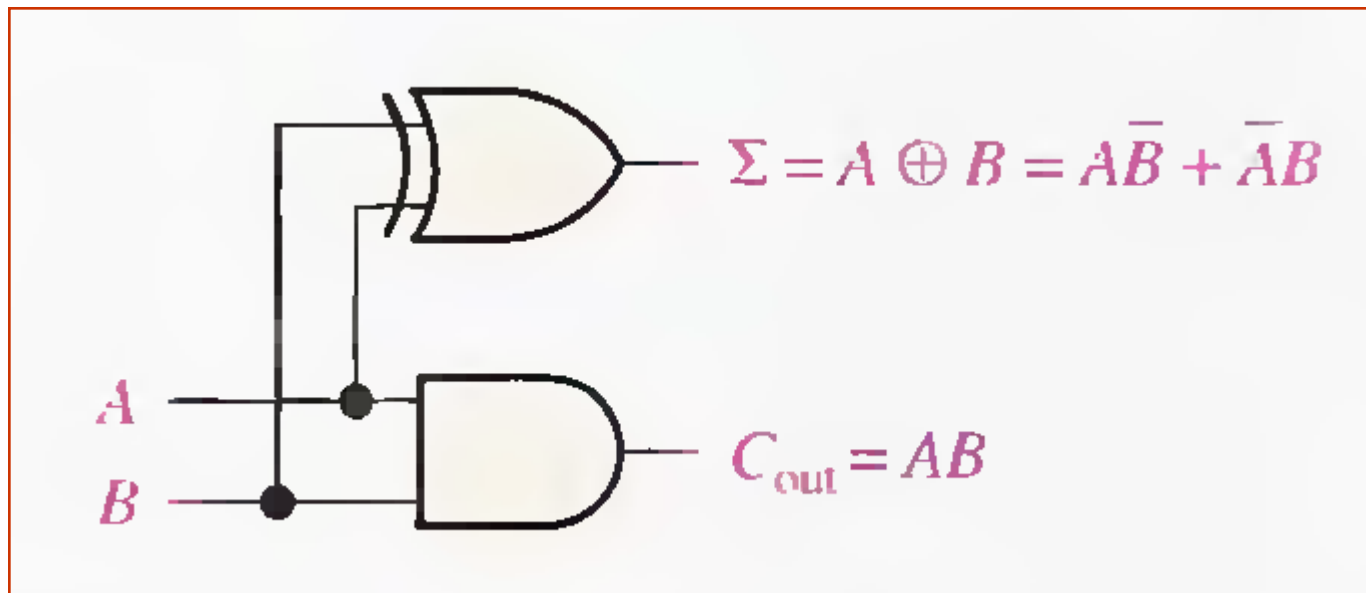

# Solutions

 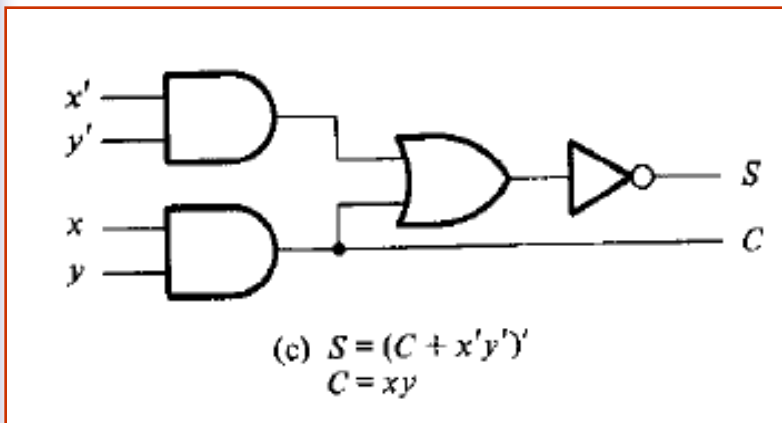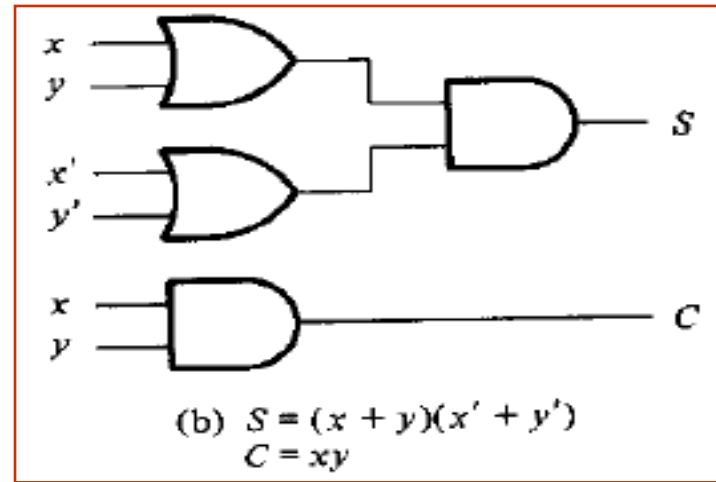 


## ■ Full Adder

- The second category of adder is the full-adder.
- The full-adder accepts two input bits and an input carry and generates a sum output and an output carry.
- The basic difference between a full-adder and a half-adder is that the full-adder accepts an input carry.



# Full Adder

- Logical symbol for full adder is,

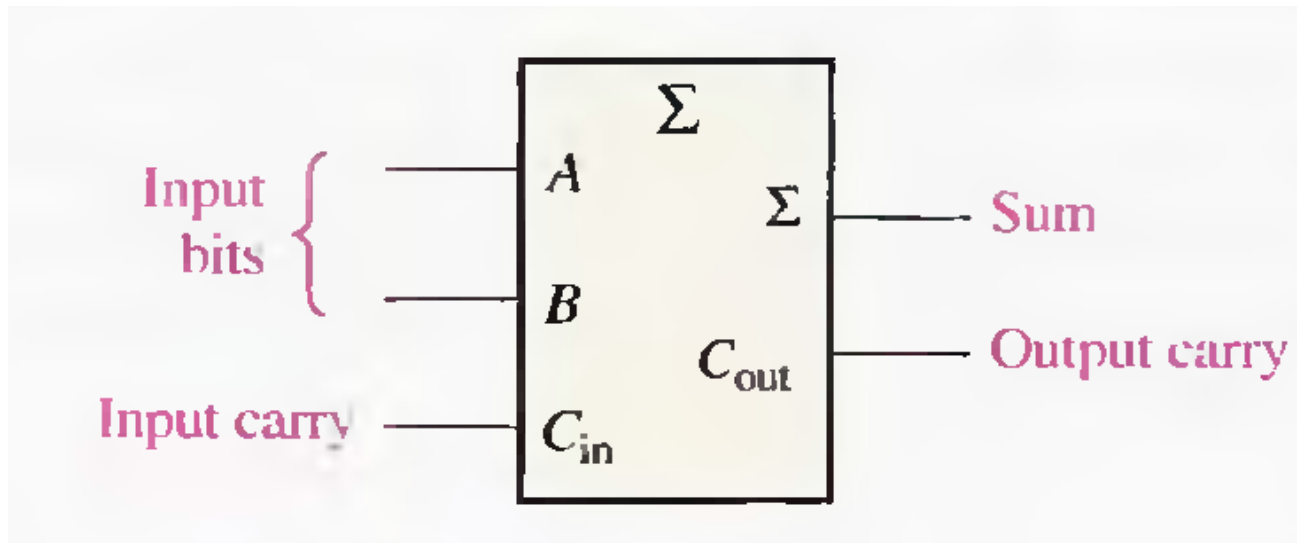



## Truth Table

$A$	$B$	$C_{in}$	$C_{out}$	$\Sigma$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$C_{in}$  = input carry, sometime designated as  $C_I$

$C_{out}$  = output carry sometimes designated as  $C_O$

$\Sigma$ =sum

$A$  and  $B$  = input variables (operands)

## ■ Full Adder Logic

- The full-adder must add the two input bits and the input carry.
- From the half-adder you know that the sum of the input bits A and B is the exclusive-OR of those two variables, A xor B.
- For the input carry ( $C_{in}$ ) to be added to the input bits. it must be exclusive-ORed with A xor B, yielding the equation for the sum output of the full-adder.

$$\Sigma = (A \oplus B) \oplus C_{in}$$

- Map for Full Adder (For Sum Function)

		<b>yz</b>			
		00	01	11	10
<b>x</b>	0		1		1
	1	1		1	


$$S = x'y'z + x'yz' + xy'z' + xyz$$

## For Carry Simplified Expression

		yz			
		00	01	11	10
x	0			1	
	1		1	1	1

$$C = xy + xz + yz$$


# Implementation of Full Adder in SOP

 

**Logic Diagram**

# Implementation of Full Adder
 
## Implementation of a full adder with two half adders and an OR Gate




$$\begin{aligned}S &= z \oplus (x \oplus y) \\&= z'(xy' + x'y) + z(xy' + x'y)' \\&= z'(xy' + x'y) + z(xy + x'y') \\&= xy'z' + x'yz' + xyz + x'y'z\end{aligned}$$


$$C = z(xy' + x'y) + xy = xy'z + x'yz + xy$$
 
# Problem


- For each of the three full-adders in Figure below, determine the outputs for the inputs shown.



(a)

 

(b)

 

(c)



(a) The input bits are  $A = 1$ ,  $B = 0$ , and  $C_{in} = 0$ .

$$1 + 0 + 0 = 1 \text{ with no carry}$$

Therefore,  $\Sigma = 1$  and  $C_{out} = 0$ .

(b) The input bits are  $A = 1$ ,  $B = 1$ , and  $C_{in} = 0$ .

$$1 + 1 + 0 = 0 \text{ with a carry of } 1$$


Therefore,  $\Sigma = 0$  and  $C_{out} = 1$ .


(c) The input bits are  $A = 1$ ,  $B = 0$ , and  $C_{in} = 1$ .


$$1 + 0 + 1 = 0 \text{ with a carry of } 1$$

Therefore,  $\Sigma = 0$  and  $C_{out} = 1$ .

# Quiz

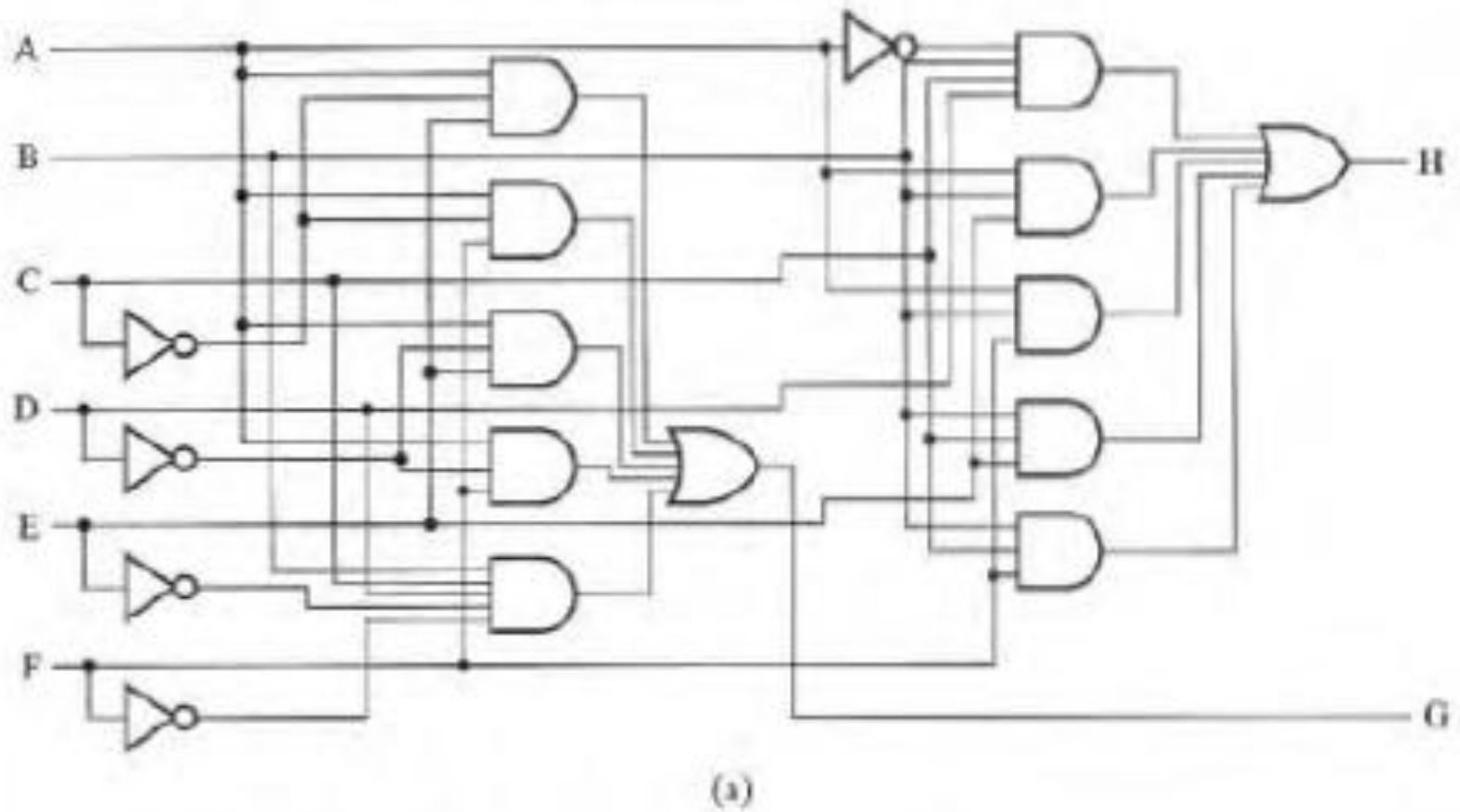

 

 

# Parallel Binary Adders

- Two or more full-adders are connected to form parallel binary adders.
- a single full-adder is capable of adding two 1-bit numbers and an input carry.
- To add binary numbers with more than one bit, you must use additional full-adders.
- When one binary number is added to another, each column generates a sum bit and a 1 or 0 carry bit to the next column to the left.



$$\begin{array}{r} 1 \\ 11 \\ + 01 \\ \hline 100 \end{array}$$

In this case, the carry bit from second column becomes a sum bit.

# Parallel Binary Adder


- To add two binary numbers, a full-adder is required for each bit in the numbers.
- So for 2-bit numbers, two adders are needed.
- For 4-bit numbers, four adders are used; and so on.
- The carry output of each adder is connected to the carry input of the next higher-order adder.
- Notice that either a half-adder can be used
- for the least significant position or the carry input of a full-adder can be made 0 (grounded) because there is no carry input to the least significant bit position.


 
# Parallel Binary Adder

General format, addition of two 2-bit numbers:

$$\begin{array}{r} A_2A_1 \\ + B_2B_1 \\ \hline \Sigma_3\Sigma_2\Sigma_1 \end{array}$$






# Parallel Binary Adder

- In Figure the least significant bits (LSB) of the two numbers are represented by  $A_1$  and  $B_1$ .
- The next higher-order bits are represented by  $A_2$  and  $B_2$  .
- The three sum bits are  $\Sigma_1, \Sigma_2$  and  $\Sigma_3$ .
- Notice that the output carry from the left-most full-adder becomes the most significant bit (MSB) in the sum,  $\Sigma_3$ .



 
# Example

- Determine the sum generated by the 3-bit parallel adder and show the intermediate carries when the binary numbers 101 and 011 are being added.



 
# Four Bit Parallel Adder

- A group of four bits is called a nibble.
- A basic 4-bit parallel adder is implemented with four full-adder stages as shown in Figure .


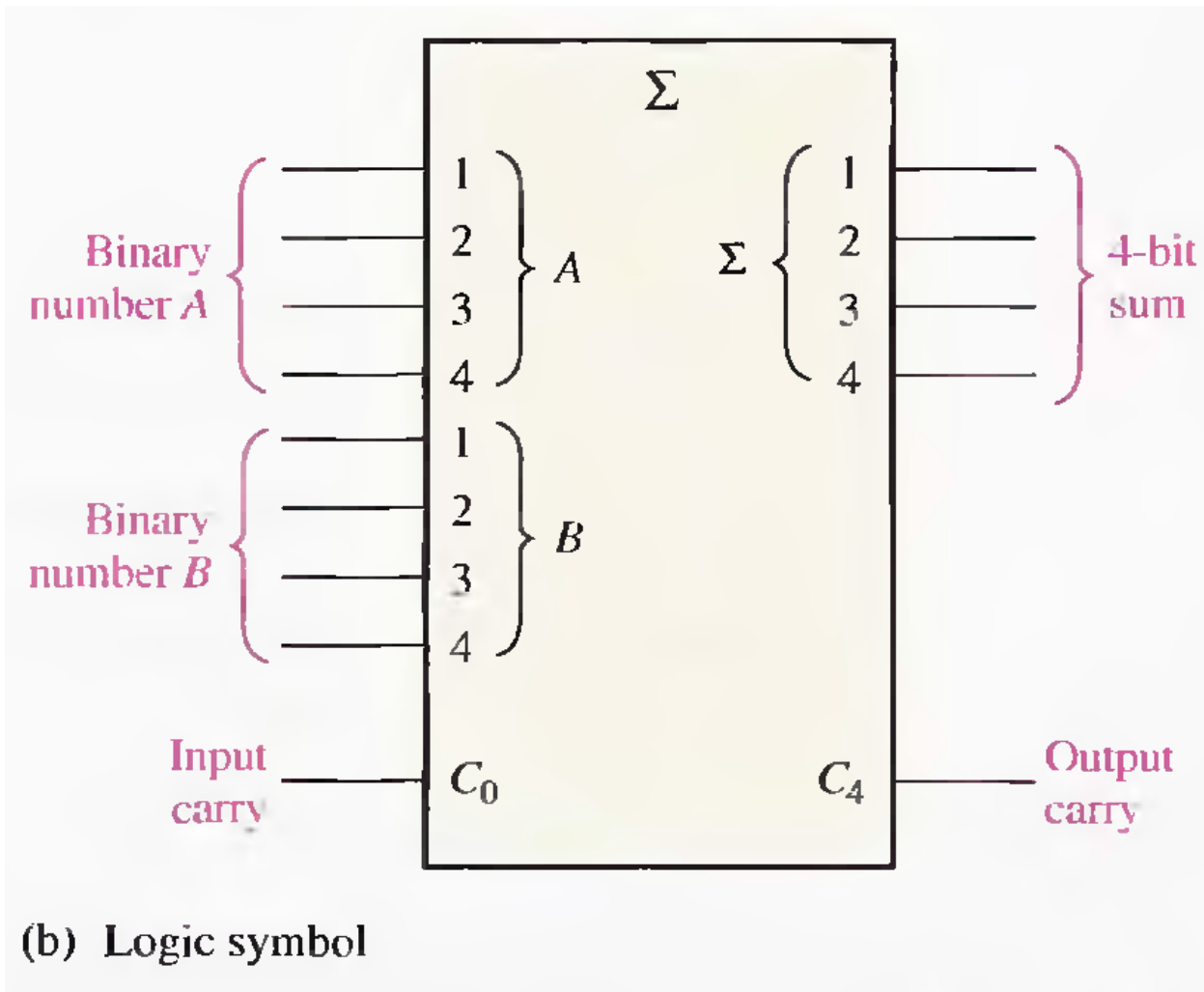
# Logical Symbol for 4 bit Parallel Adder




# 4 bit parallel adder

- The input labeled  $C_0$  is the input carry to the least significant bit adder.
- $C_4$  in the case of four bits, is the output carry of the most significant bit adder; and  $\Sigma_1$  (LSB) through  $\Sigma_4$  (MSB) are the sum outputs.
- The 4-bit parallel adder can be expanded to handle the addition of two 8-bit numbers by using two 4-bit adders.



# 8 Bit Adder

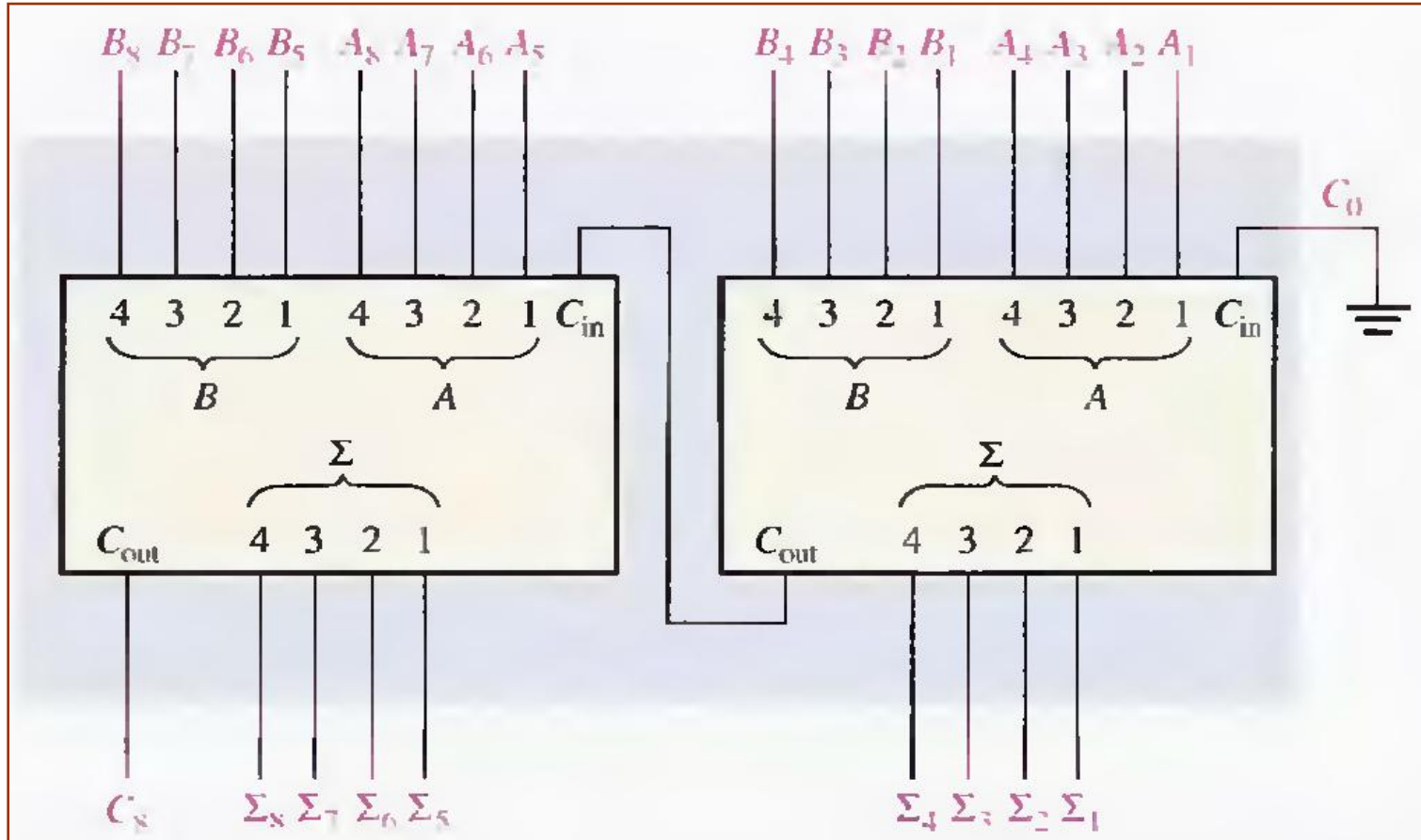

**Cascading of two 4-bit adders to form an 8-bit adder**

# Subtractors

- Subtraction of two binary number is accomplished by taking the complement of the subtrahend and adding it to the minuend.
- Logically it can be done through direct method.
- In this method each bit of the subtrahend is subtracted from its corresponding significant minuend bit to form a difference bit.
- If the minuend bit is smaller then a 1 borrow is taken from the next higher pair of the bits.



## ■ Half Subtractor

- It subtract two bits and produces their difference.
- It also has an output to specify if a 1 has been borrowed.
- $x$  and  $y$  are minuend and subtrahend variable.
- For subtraction we check the relative magnitude of the  $x$  and  $y$ .
- If  $x \geq y$  then no issue.
- If  $x < y$  then it is necessary to take a borrow from the next higher stage.



# Half subtractor

- Truth table of half subtractor is,

<b>X</b>	<b>Y</b>	<b>B</b>	<b>D</b>
0	0	0	0
0	1	1	1
1	0	0	1
1	1	0	0

$$D = x' y + x y'$$

$$B = x' y$$

# Problem

- Draw a circuit diagram against Difference  $D$  and Borrow  $B$ .



# Full Subtractor

- It performs a subtraction between two bits, taking in to account that a 1 may have been borrowed by a lower significant stage.
- It has three inputs and two outputs.
- Three inputs  $x$ ,  $y$  and  $z$  shows the minuend, subtrahend and previous borrow respectively.
- $B$  and  $D$  represents the output borrow and Difference.



# Full Subtractor

- Truth table is as under,

$x$	$y$	$z$	$B$	$D$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

# Full Subtractor

- The function against B and D are,

$$D = x'y'z + x'yz' + xy'z' + xyz$$

$$B = x'y + x'z + yz$$

		yz	y		
	x	00	01	11	10
	0		1		1
	1	1		1	
		z			

$$D = x'y'z + x'yz' + xy'z' + xyz$$

			y		
	x	00	01	11	10
	0		1	1	1
	1			1	
		z			

$$B = x'y + x'z + yz$$

# Code conversion





- Some times the output of the one system as the input to another.
- If both the system uses different coding system, then code convertor is needed between them.
- Thus a code convertor is a circuit that makes the two system compatible.
- To convert from binary code A to B,
  - Input lines supply the bit combination of elements by Code A and the output lines must generate the corresponding bit combination for code B.

- Code conversion from BCD to Excess 3 is illustrated below,

- 1) BCD code: ABCD
- 2) Excess-3 code: WXYZ
- 3) Truth table:


Decimal	A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0
10	1	0	1	1	x	x	x	x
⋮	⋮	⋮	⋮	⋮	⋮	⋮	⋮	⋮
15	1	1	1	1	x	x	x	x

# Outputs Simplification

 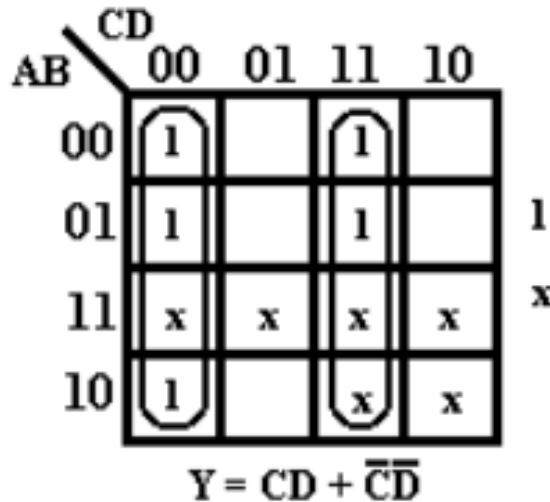  





# Circuit Diagram

 

# Binary to Gray code

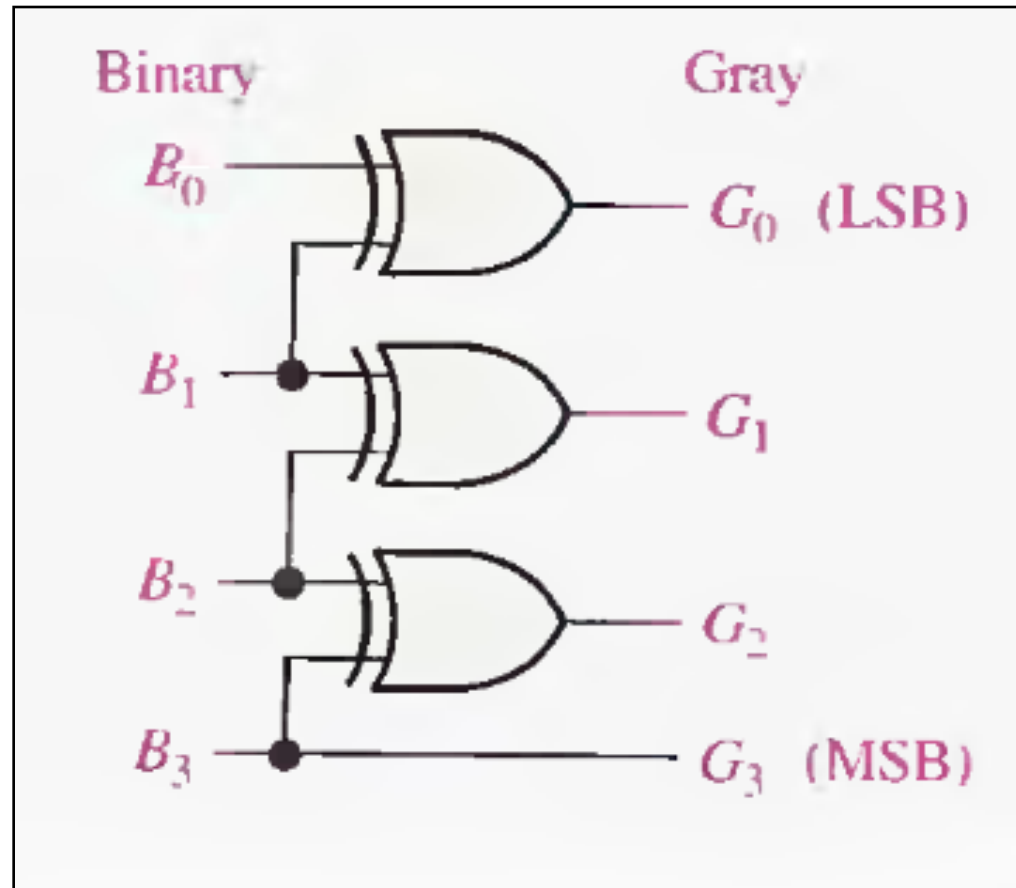

# Gray to Binary

 

## Related Problem

How many exclusive-OR gates are required to convert 8-bit binary to Gray?



