



Karnaugh Maps Simplification

Rab Nawaz Khan Jadoon

Lecturer

COMSATS Lahore

Pakistan

Department of Computer Science

DCS

COMSATS Institute of
Information Technology

Digital Logic and Computer Design

K-Map Simplification

- After an SOP expression has been mapped, a minimum SOP expression is obtained by grouping the 1s and determining the minimum SOP expression from the map.
- You can group 1s on the Karnaugh map according to the following rules by enclosing those adjacent cells containing 1s.
- The goal is to maximize the size of the groups and to minimize the number of groups.

- **Karnaugh map** is an array of cells in which each cell represents a binary value of the input variables.
- The cells are managed in a way so that simplification of a given expression is simply a matter of properly grouping the cells.
- **Karnaugh maps** can be used for expressions with two, three, four, and five variables, but we will discuss only 3-variable and 4-variable situations to illustrate the principles.

■ Steps for Grouping

- A group must contain either 1, 2, 4, 8, or 16 cells, which are all powers of two. In the case of a 3-variable map, $2^3 = 8$ cells is the maximum group.
- Each cell in a group must be adjacent to one or more cells in that same group. but all cells in the group do not have to be adjacent to each other.
- Always include the largest possible number of 1's in a group in accordance with rule 1.
- Each 1 on the map must be included in at least one group. The 1s already in a group can be included in another group as long as the overlapping groups include noncommon 1's.

For Example


$AB \backslash C$	0	1
00	1	
01		1
11	1	1
10		

$AB \backslash C$	0	1
00	1	
01		1
11	1	1
10		

Example

Wrap around adjacency

$AB \backslash C$	0	1
00	1	1
01	1	
11		1
10	1	1

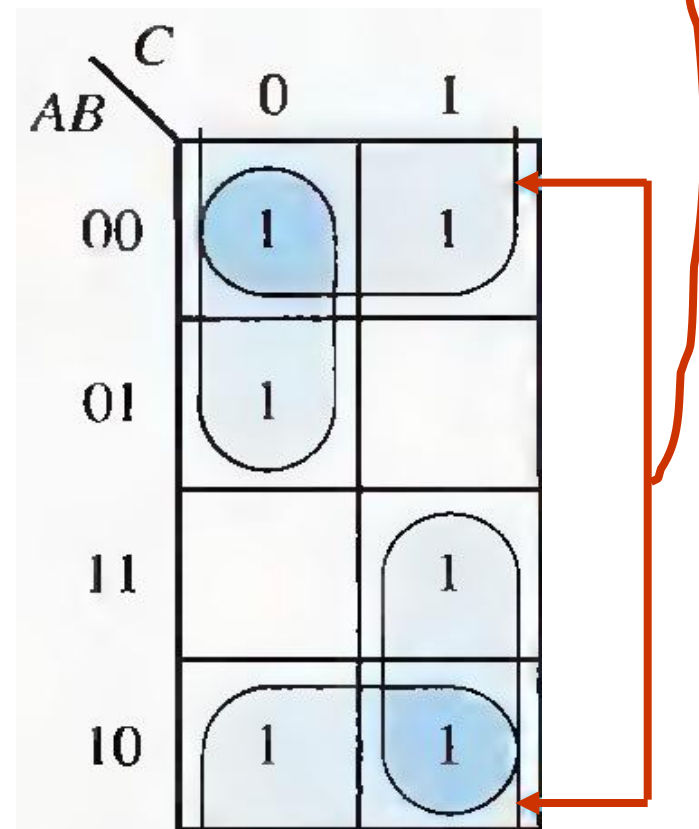

K-Maps


$AB \backslash CD$	00	01	11	10
00	1	1		
01	1	1	1	1
11				
10		1	1	

$AB \backslash CD$	00	01	11	10
00	1	1		
01	1	1	1	1
11				
10		1	1	

K-Maps

Wrap around adjacency

<i>AB</i> \ <i>CD</i>	00	01	11	10
00	1			1
01	1	1		1
11	1	1		1
10	1		1	1

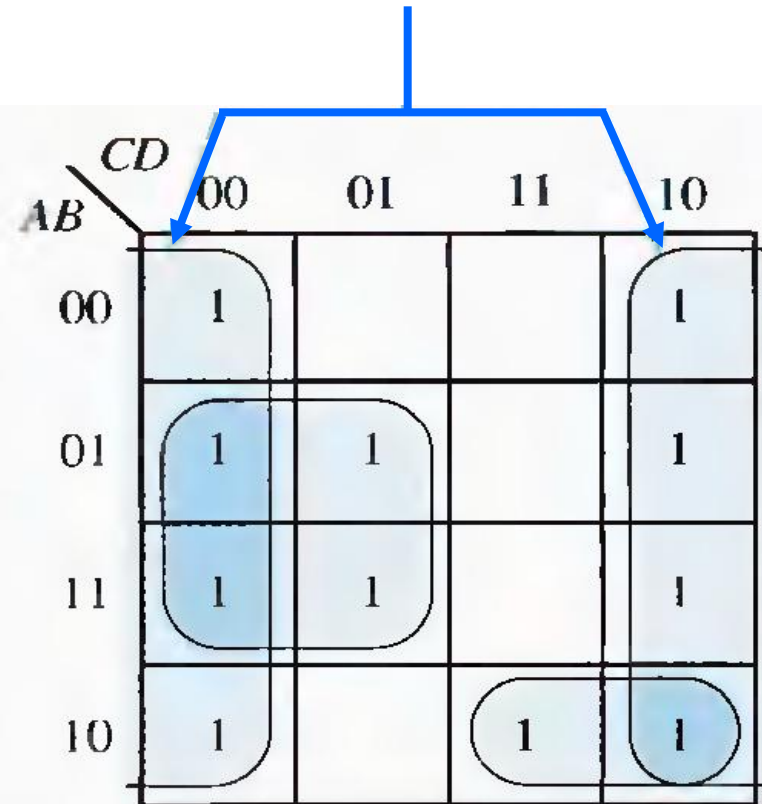

- **Determining the Minimum SOP Expression from the Map.**
 - When all the 1's representing the standard product terms in an expression are properly mapped and grouped, the process of determining the resulting minimum SOP expression begins.
 - **Rules**
 - Group the cells that have 1's. Each group of cells containing 1s creates one product term composed of all variables that occur in either form within the group.
 - Variables that occur both uncomplemented and complemented within the group are eliminated. These are called contradictory variables.

The 4-Variable Karnaugh Map

- Determining the minimum term for each group

- For a 3-variable map.

- (1) A 1-cell group yields a 3-variable product term
- (2) A 2-cell group yields a 2-variable product term
- (3) A 4-cell group yields a 1-variable term
- (4) An 8-cell group yields a value of 1 for the expression

- For a 4-variable map

- (1) A 1-cell group yields a 4-variable product term
- (2) A 2-cell group yields a 3-variable product term
- (3) A 4-cell group yields a 2-variable product term
- (4) An 8-cell group yields a 1-variable term
- (5) A 16-cell group yields a value of 1 for the expression

Note: When all the minimum product terms are derived from the Karnaugh map, they are summed to form the minimum SOP expression.


Related Example

- Minimize the following SOP expression,
 - $F(x, y, z) = \Sigma(0,2,6,7)$ → 1
 - $F(x, y, z) = \Sigma(0,2,3,4,6)$ → 2
 - $F(x, y, z) = \Sigma(0,1,2,3,7)$ → 3
 - $F(x, y, z) = \Sigma(3,5,6,7)$ → 4
 - $F(x, y, z) = \Sigma(0,1,5,7)$ → 5
 - $F(x, y, z) = \Sigma(0,1,6,7)$ → 6
 - $F(x, y, z) = \Sigma(1,2,3,6,7)$ → 7



Solution

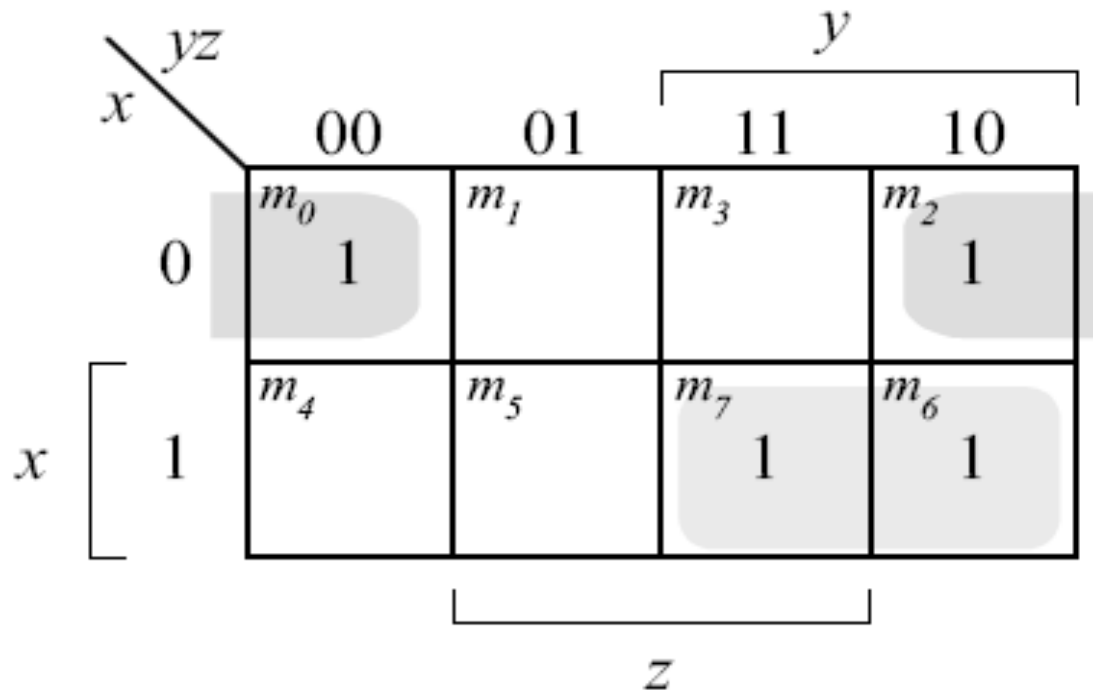■ $F(x, y, z) = \Sigma(0,2,6,7) \rightarrow 1$



$$F = x y + x' z'$$

■ Solution


$$F(x, y, z) = \Sigma(0,2,3,4,6) \quad \rightarrow \quad 2$$

		y			
		00	01	11	10
x	0	m_0 1	m_1	m_3 1	m_2 1
	1	m_4 1	m_5	m_7	m_6 1
		z			

$$F = z' + x'y$$

■ Solution

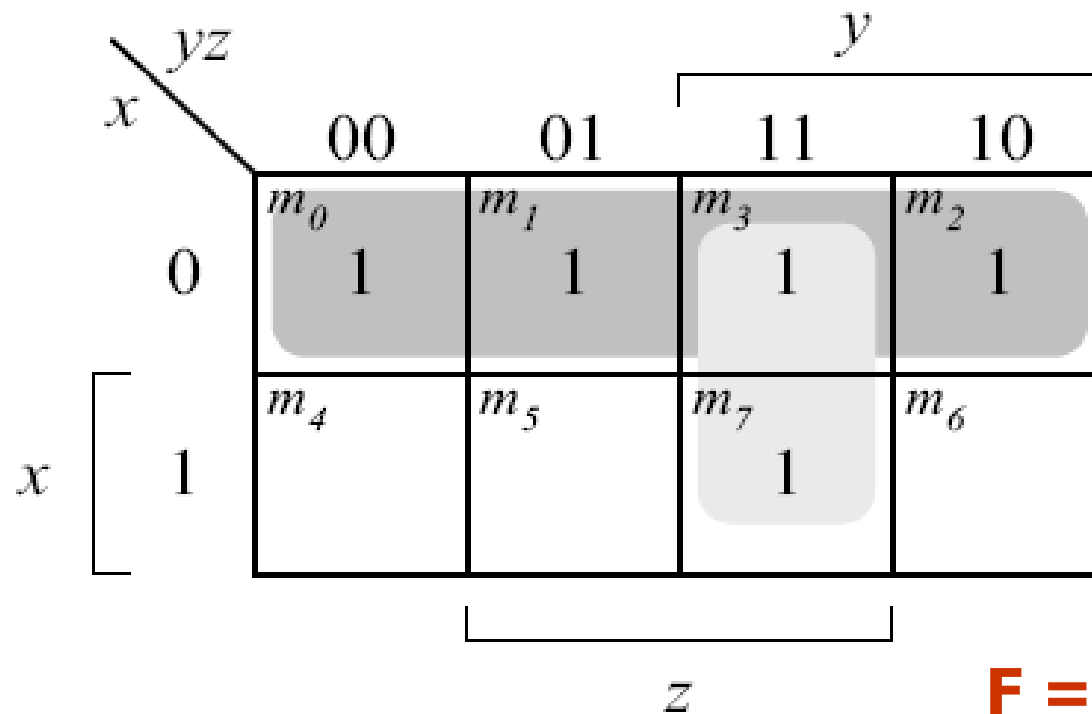
$$F(x, y, z) = \Sigma(0,1,2,3,7) \quad \rightarrow \quad 3$$



$$F = x' + yz$$

■ Solution
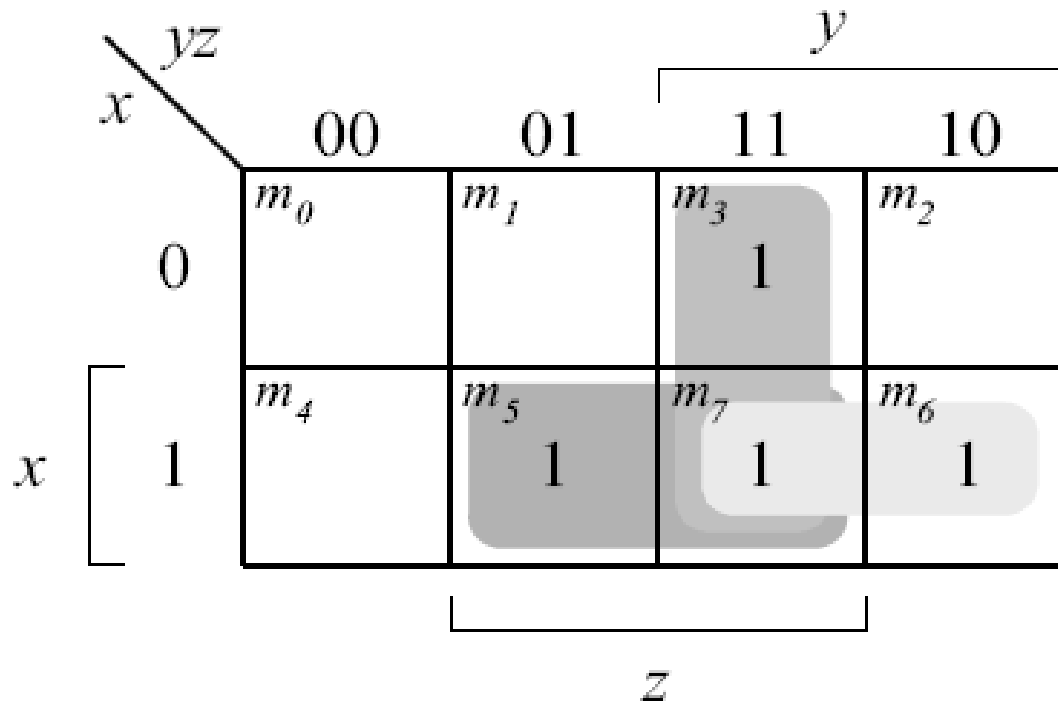
$$F(x, y, z) = \Sigma(3,5,6,7) \quad \rightarrow \quad 4$$



$$F = xy + xz + yz$$

Solution of 5, 6, 7

		y			
		00	01	11	10
x	yz				
	x	0	1	1	1
0	m ₀	m ₁	m ₃	m ₂	
1	m ₄	m ₅	m ₇	m ₆	

$$5. F = x' y' + x z$$

		y			
		00	01	11	10
x	yz				
	x	0	1	1	1
0	m ₀	m ₁	m ₃	m ₂	
1	m ₄	m ₅	m ₇	m ₆	

$$6. F = x' y' + x y$$

		y			
		00	01	11	10
x	yz				
	x	0	1	1	1
0	m ₀	m ₁	m ₃	m ₂	
1	m ₄	m ₅	m ₇	m ₆	

$$7. F = y + x' z$$


■ Example

- Determine the product terms for the Karnaugh map given and write the resulting minimum SOP expression?

		<i>CD</i>			
		00	01	11	10
<i>AB</i>	00			1	1
	01	1	1	1	1
	11	1	1	1	1
	10		1		

■ Solution

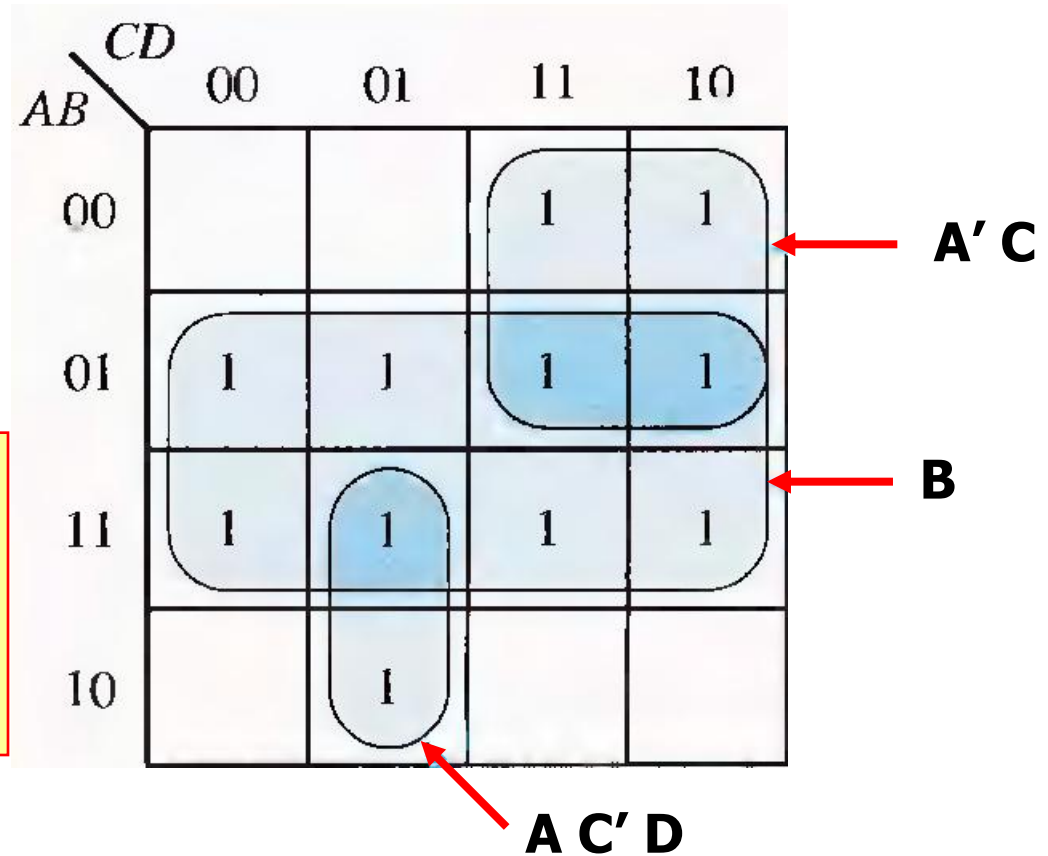The resulting minimum SOP expression is,
 $B + A' C + A C' D$
 the sum of these product terms:



Self Assessment

Problem: For the Karnaugh map on the previous slide, add a 1 in the lower right cell (1010) and determine the resulting SOP expression.



Example 1

$AB \backslash C$	0	1
00	1	
01		1
11	1	1
10		

a

$AB \backslash CD$	00	01	11	10
00	1	1		
01	1	1	1	1
11				
10		1	1	

b

Example 2

$AB \backslash C$	0	1
00	1	1
01	1	
11		1
10	1	1

c

$AB \backslash CD$	00	01	11	10
00	1			1
01	1	1		1
11	1	1		1
10	1		1	1

d

- The resultant SOP expression against a, b, c and d are,
 - a. $AB+BC+A' B' C'$
 - b. $A' B + A' C' + AB' D$
 - c. $B' + A' C' + AC$
 - d. $D' + AB' C + BC'$

Class Assignment

- Using k-map simplify the following expression,

$$F(A,B,C,D) = \Sigma(0,2,3,4,6,8,10,11,12,14)$$

Just do it in 3min. Only.




The resulting minimum SOP expression is

$$\mathbf{D' + B' C}$$

- Find the minimized SOP expression against the following,
 1. $F(A,B,C,D) = \Sigma(4,6,7,15)$
 2. $F(A,B,C,D) = \Sigma(3,7,11,13,14,15)$
 3. $F(A,B,C,D) = \Sigma(0,1,5,8,9)$
 4. $F(A,B,C,D) = \Sigma(1,4,5,6,12,14,15)$

■ Solution
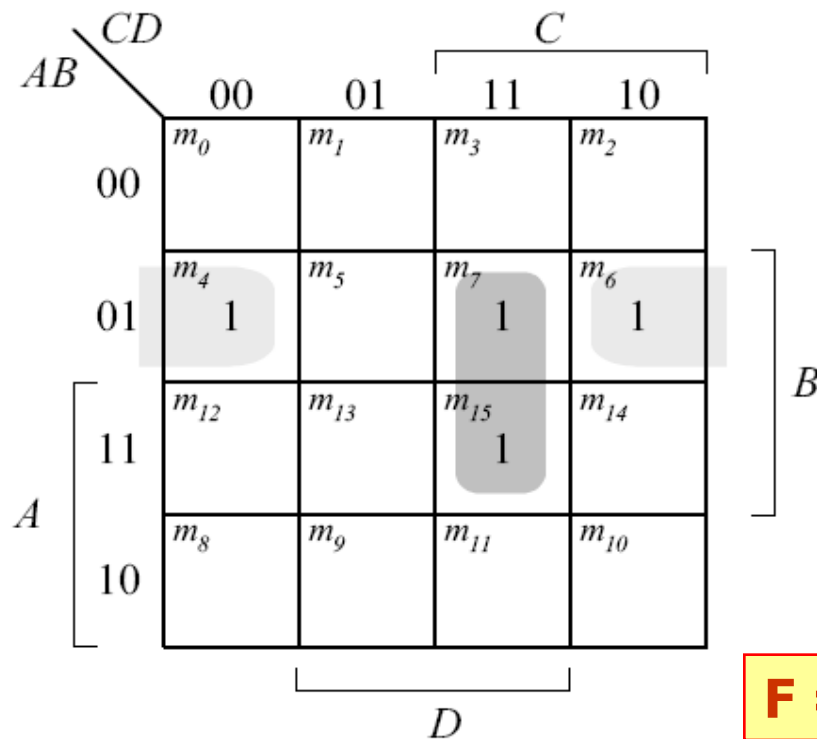
$$1. F(A, B, C, D) = \Sigma(4, 6, 7, 15)$$



$$F = BCD + A' BD'$$

Solution

$$2. F(A,B,C,D) = \Sigma(3,7,11,13,14,15)$$


AB		CD			
		00	01	11	10
A	00	m_0	m_1	m_3 1	m_2
	01	m_4	m_5	m_7 1	m_6
	11	m_{12}	m_{13} 1	m_{15} 1	m_{14} 1
	10	m_8	m_9	m_{11} 1	m_{10}

Diagram illustrating the Karnaugh map for the function $F(A,B,C,D) = \Sigma(3,7,11,13,14,15)$. The map is a 4x4 grid with rows labeled AB (00, 01, 11, 10) and columns labeled CD (00, 01, 11, 10). The cells are labeled m_0 through m_{15} . The function is represented by 1s in the cells $m_3, m_7, m_{11}, m_{13}, m_{14}, m_{15}$. The map is partitioned into groups: a vertical group of 2 cells (m_3, m_7) labeled C, a horizontal group of 3 cells (m_{13}, m_{15}, m_{14}) labeled B, and a vertical group of 2 cells (m_{13}, m_{11}) labeled D.

$$F = CD + ABD + ABC$$

Solution


$$3. F(A,B,C,D) = \Sigma(0,1,5,8,9)$$

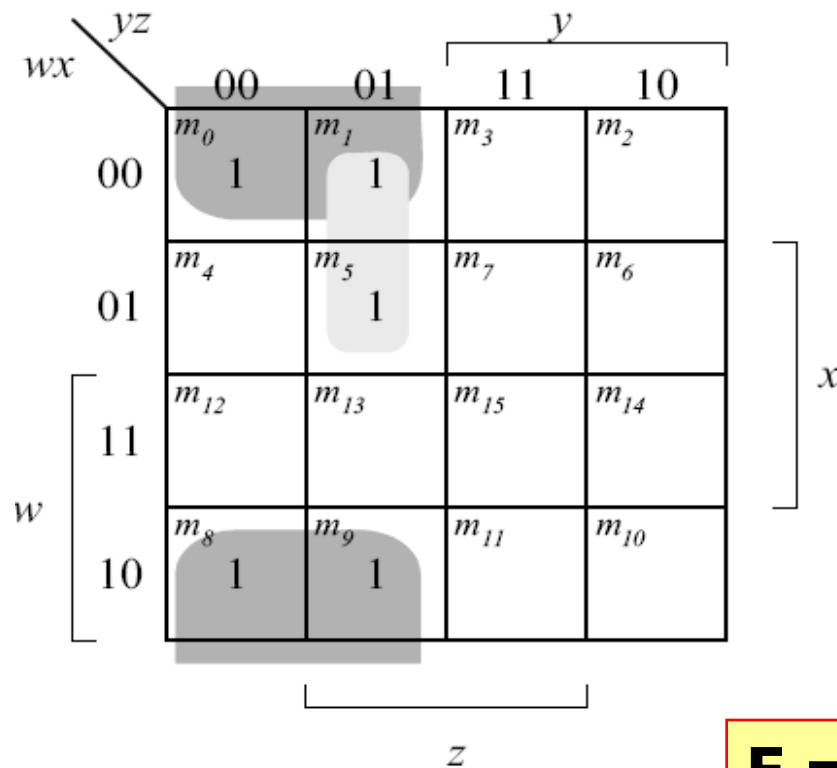

$$F = x'y' + w'y'z$$

■ Solution
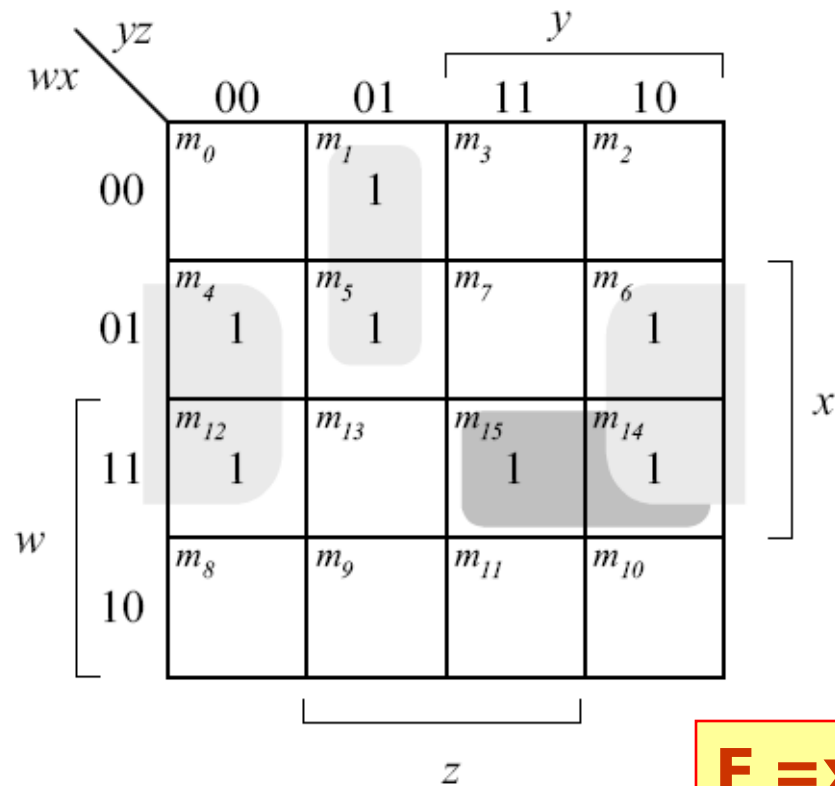
$$4. F(A,B,C,D) = \Sigma(1,4,5,6,12,14,15)$$



$$F = xz' + w'y'z + wxy$$

Assignment# 2

- Simplify the following SOP Expression,
 1. $F(A,B,C,D) = \Sigma(1,2,3,5,7,9,10,11,13,15)$
 2. $F(A,B,C,D) = \Sigma(1,2,3,5,9,10,11,12,13)$
 3. $F(A,B,C,D) = \Sigma(0,2,3,5,7,8,10,11,14,15)$
 4. $F(A,B,C,D) = \Sigma(2,3,7,10,11,12,13,14,15)$
 5. $F(A,B,C,D) = \Sigma(1, 3, 5, 9, 12, 13, 14)$
 6. $F(A,B,C,D) = \Sigma(0, 2, 4,5,6,7, 8, 10, 13, 15)$


Due date: Next Incoming Class
No Copy/Past Material should be,



NAND and NOR Implementation




AND-invert

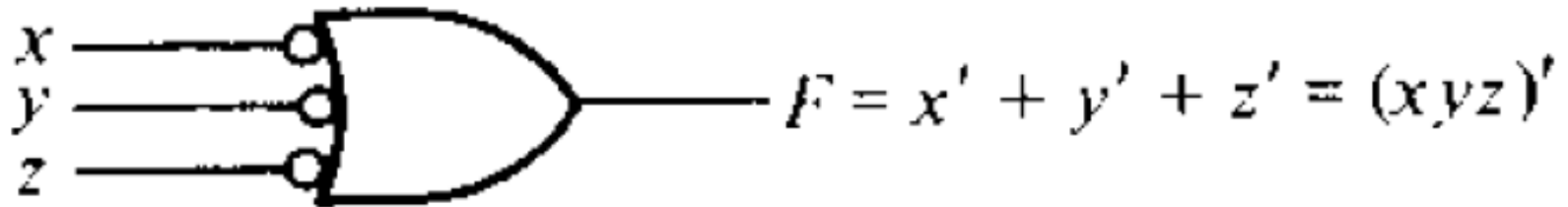


Invert-OR

NOR Equivalent

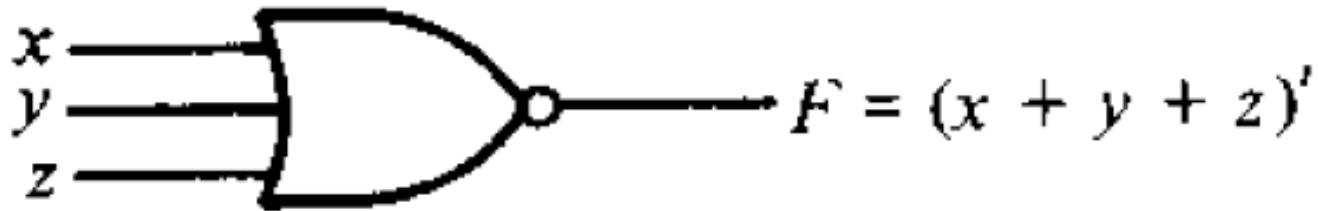


OR-invert

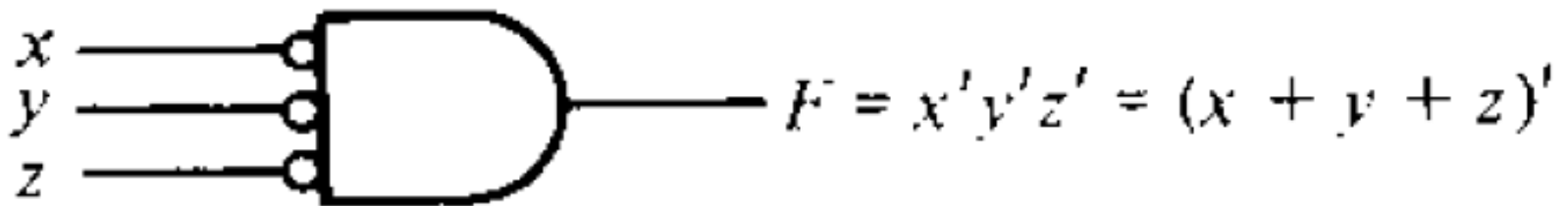


Invert-AND

NAND Implementation


$$F = AB + CD + E$$

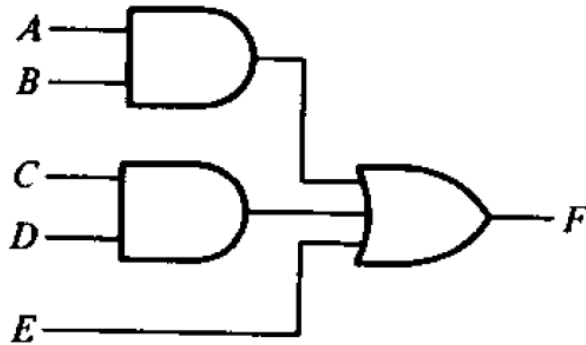

AND-OR

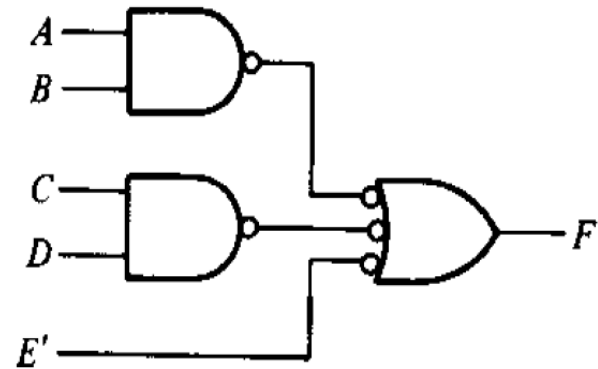

NAND-NAND

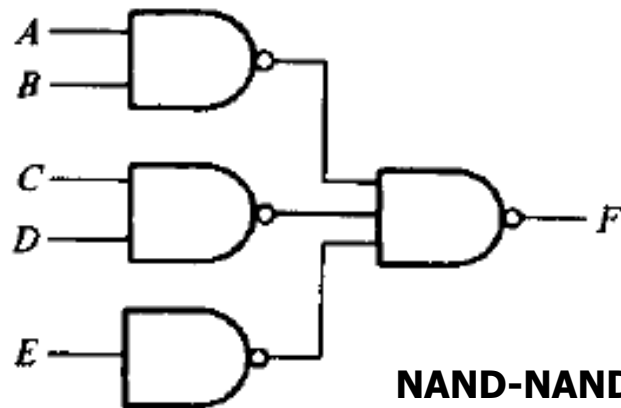


NAND-NAND

NAND implementation


- Implement the following function using NAND,
 $F(x, y, z) = \Sigma(0, 6)$

x \ yz	00	01	11	10
0	1	0	0	0
1	0	0	0	1
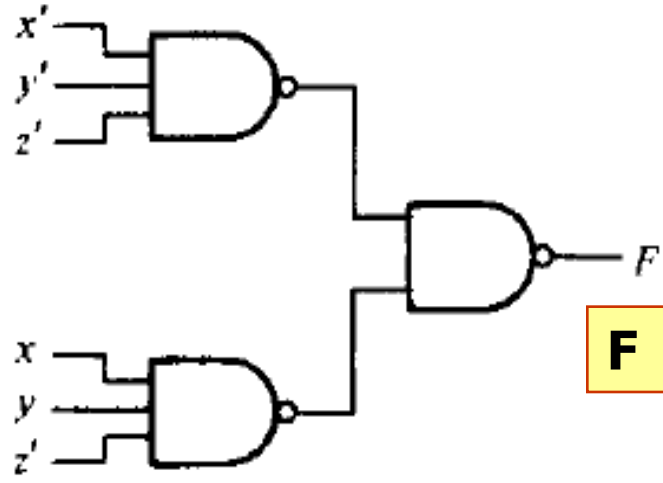
$$F = x' y' z' + xyz'$$
$$F' = x' y + x y' + z$$




$$F = x' y' z' + x y z'$$

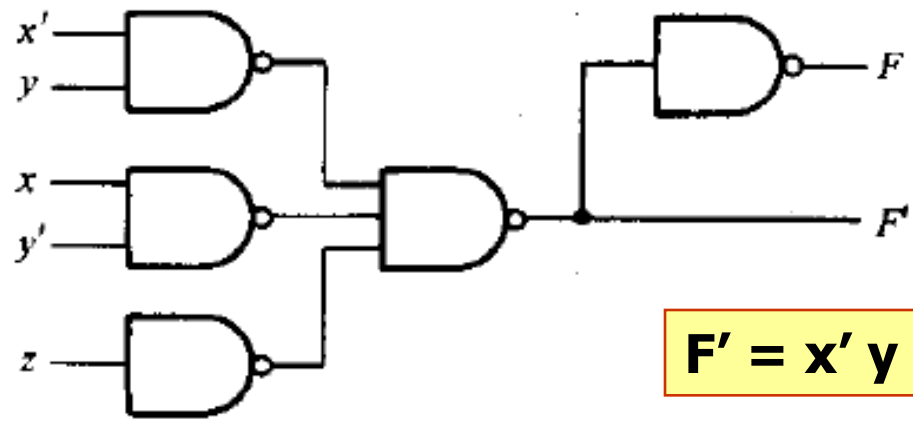


$$F' = x' y + x y' + z$$

NOR Implementation

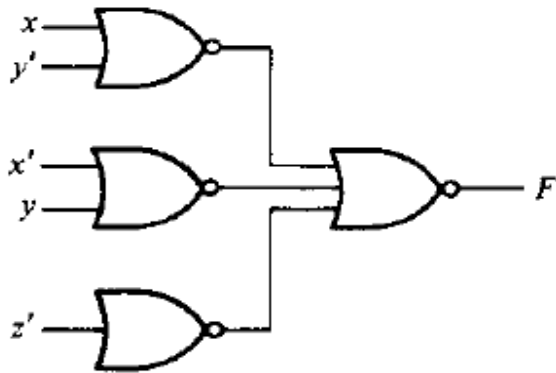- Taking the function and expand it using demorgan theorem we, get,
 - $F' = x' y + x y' + z$
 - $F = (x+y')(x'+y)z'$



$$F = (x+y')(x'+y)z'$$

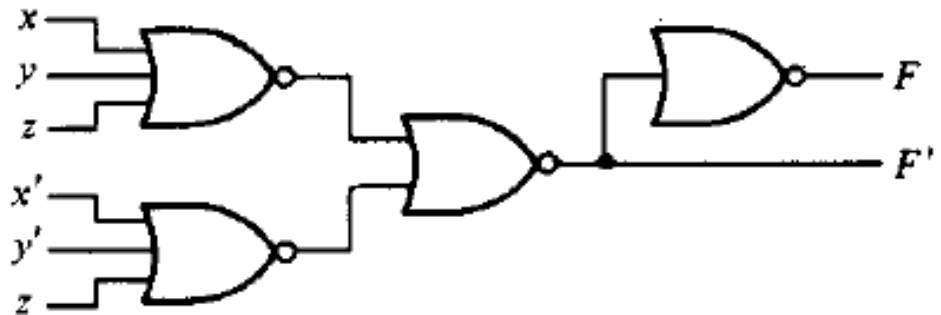


$$F = x'y'z' + xyz'$$
$$F' = (x+y+z)(x'+y'+z)$$


AND-OR-INVERT Implementation

- Let the function is


- $F = (AB + CD + E)'$

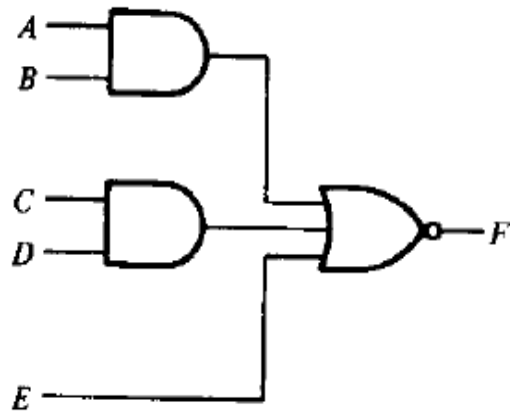

AND-NOR

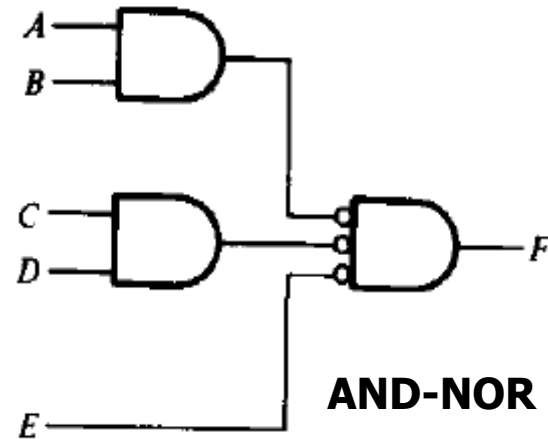


AND-NOR

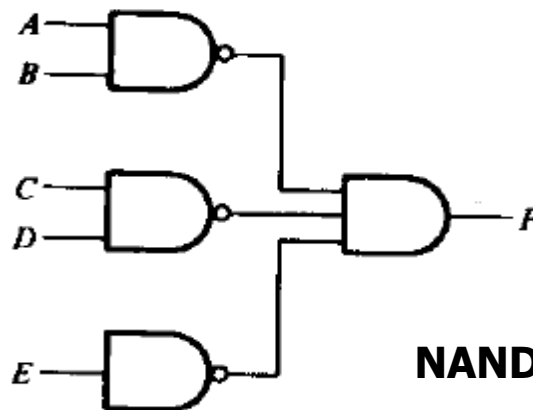


NAND-AND

OR-AND-Invert

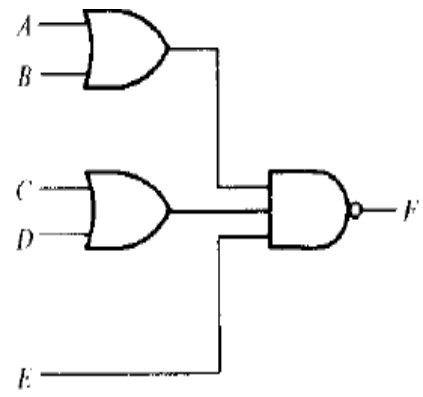
- Let the function is
 - $F = [(A+B)(C+D)E]'$



OR-NAND

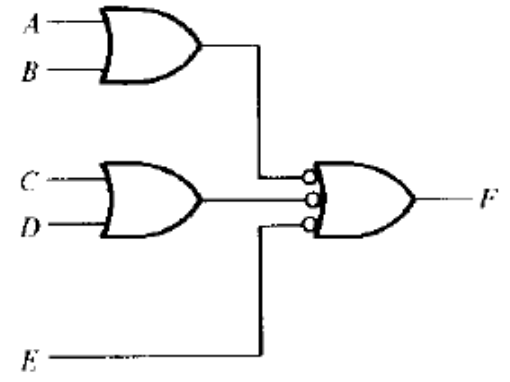

OR-NAND

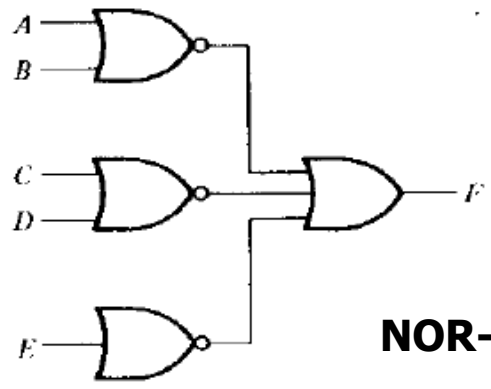

NOR-OR

DON'T care conditions

- Sometimes a situation arises in which some input variable combinations are not allowed. For example, recall that in the BCD code.
 - There are six invalid combinations: 1010, 1011, 1100, 1101, 1110, and 1111.
 - Since these unallowed states will never occur in an application involving the BCD code, they can be treated as "don't care" terms with respect to their effect on the output.
 - The "don't care" terms can be used to advantage on the Karnaugh map.





- For each "don't care" term, an X is placed in the cell.
 - When grouping the 1's, the X's can be treated as 1's to make a larger grouping or as 0's if they cannot be used to advantage.
 - The larger a group, the simpler the resulting term will be.

Inputs				Output
A	B	C	D	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

DON'T care conditions

- The truth table in Figure below describes a logic function that has a 1 output only when the BCD code for 7,8, or 9 is present on the inputs. If the "don't cares" are used as 1s, the resulting expression for the function is $A + BCD$.

Inputs ABCD	Output Y
0000	0
0001	0
0010	0
0011	0
0100	0
0101	0
0110	0
0111	1
1000	1
1001	1
1010	X
1011	X
1100	X
1101	X
1110	X
1111	X

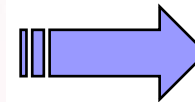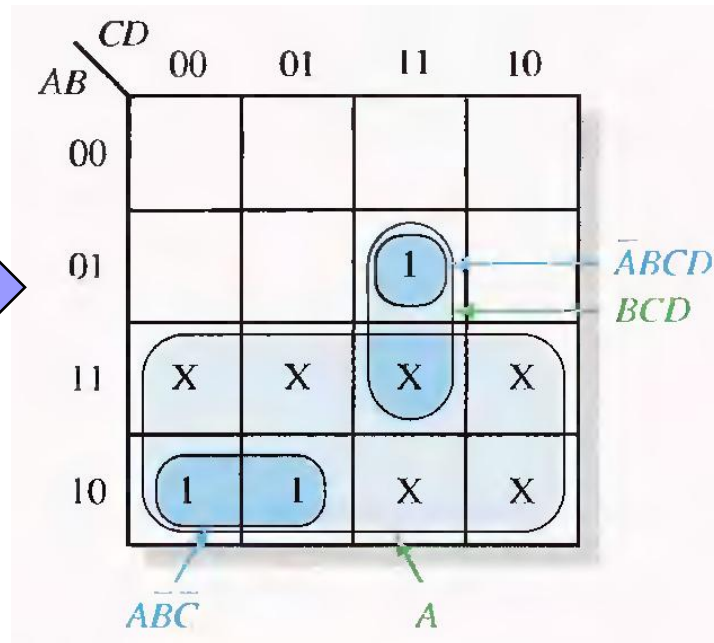

Without "don't cares"
 $Y = A'B'C'D + A'BCD$
 With "" don't cares"
 $Y = A + BCD$

Related Problem

- Simplify the Boolean functions

$$F(w,x,y,z) = \Sigma(1,3,7,11,15)$$

Don't care conditions are,

$$d(w,x,y,z) = \Sigma(0,2,5)$$

Solution

	yz			
	00	01	11	10
wx				
00	X	1	1	X
01	0	X	1	0
11	0	0	1	0
10	0	0	1	0

$$F = yz + w'x'$$

Example

		y			
		yz			
wx		00	01	11	10
w	00	X	1	1	X
	01	0	X	1	0
	11	0	0	1	0
	10	0	0	1	0

The diagram shows a 4x4 Karnaugh map for variables w, x, y, and z. The columns are labeled yz (00, 01, 11, 10) and grouped under y. The rows are labeled wx (00, 01, 11, 10) and grouped under w. The map contains 1s in the following cells: (wx=00, yz=01), (wx=00, yz=11), (wx=01, yz=11), (wx=11, yz=11), and (wx=10, yz=11). There are also Xs in the cells (wx=00, yz=00), (wx=00, yz=10), (wx=01, yz=00), and (wx=01, yz=10). Brackets indicate the groupings for y and w. A vertical bracket on the right side of the map is labeled x, indicating the vertical axis.


(b) $F = yz + w'z$

Five variable K map

- Boolean functions with five variables can be simplified using a 32-cell Karnaugh map.
- Actually, two 4-variable maps (16 cells each) are used to construct a 5-variable map.
- A Karnaugh map for five variables (ABCDE) can be constructed using two 4-variable maps with which you are already familiar.
- Each map contains 16 cells with all combinations of variables B, C, D, and E.
- One map is for A = 0 and the other is for A = 1, as shown on the next slide.



5 variable K map

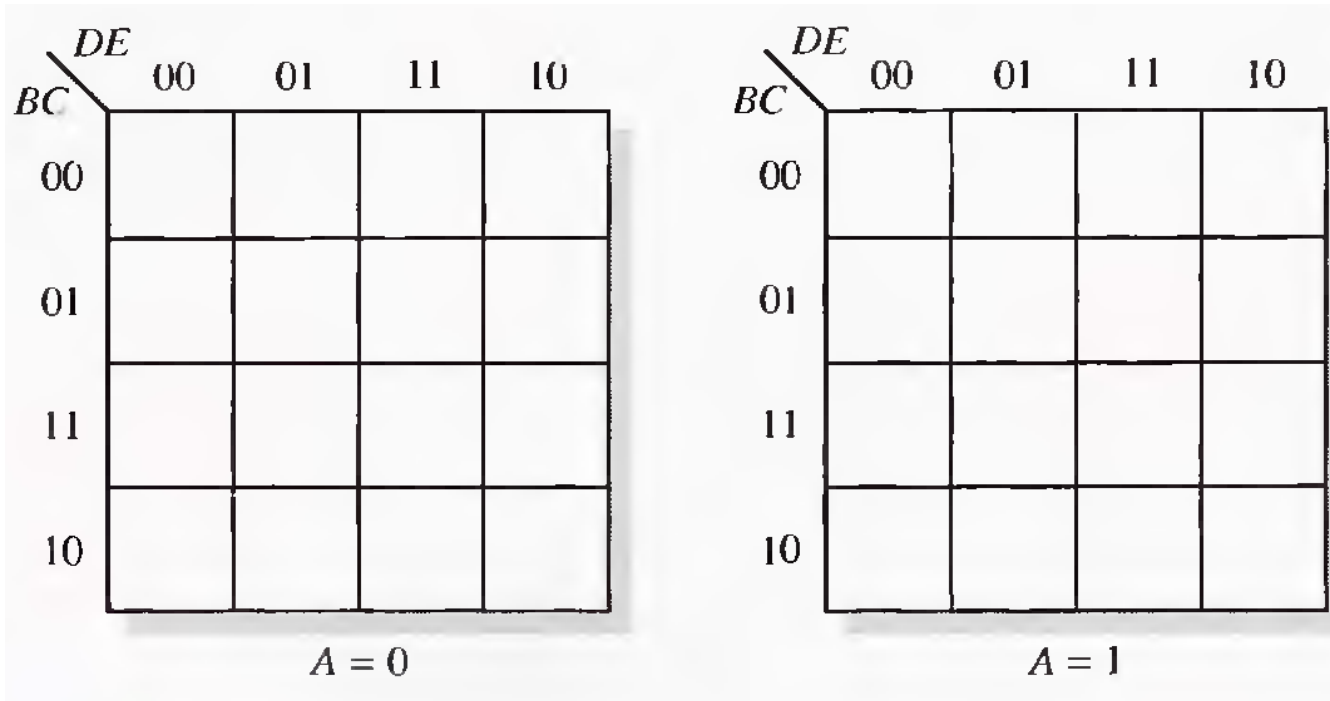


Cell Adjacency

- The best way to visualize cell adjacencies between the two 16-cell maps is to imagine that the $A = 0$ map is placed on top of the $A = 1$ map.
- Each cell in the $A = 0$ map is adjacent to the cell directly below it in the $A = 1$ map.



Cell Adjacency

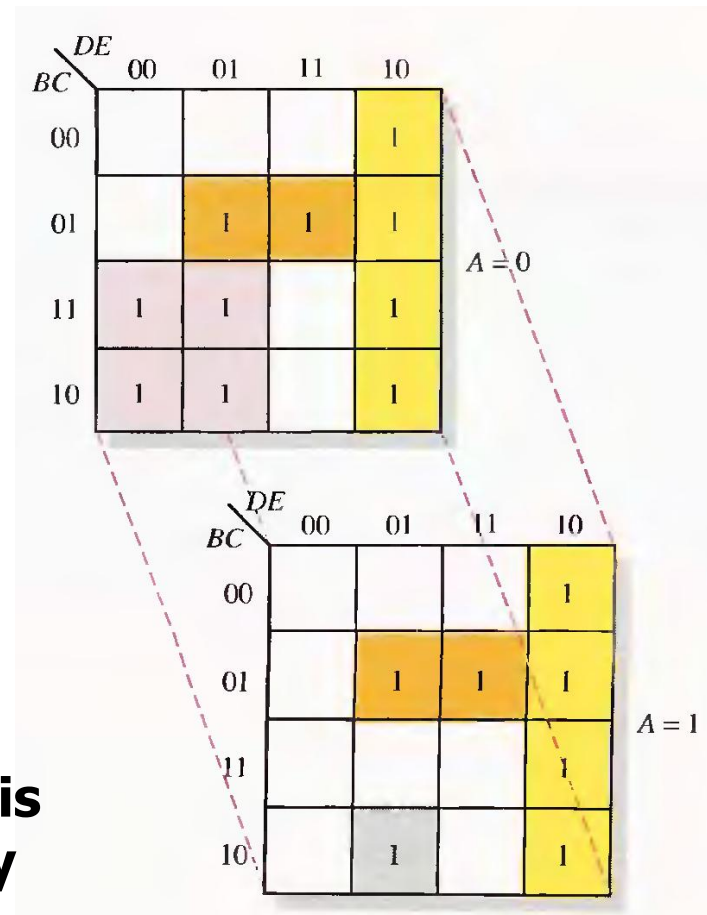

Each cell in the $A = 0$ map is adjacent to the cell directly below it in the $A = 1$ map.

5 variable K Map


- The simplified expression taken from the map is developed as follows
 - The term for the yellow group is DE' .
 - The term for the orange group is $B'CE$.
 - The term for the light red group is $A'BD'$.
 - The term for the gray cell grouped with the red cell is $BC' D'E$.
 - The final SOP expression is,
 - **$X = DE' + B'CE + A'BD' + BC' D'E$**



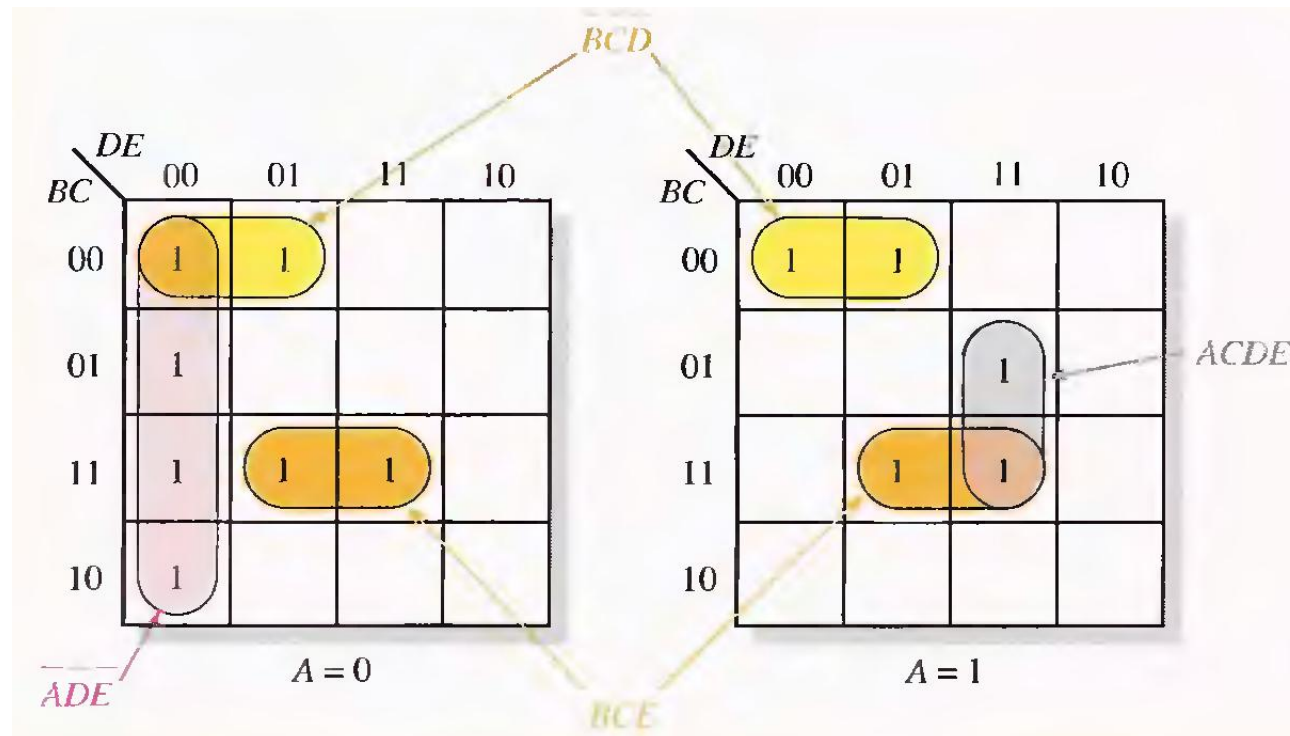Example

Use a Karnaugh map to minimize the following standard SOP 5-variable expression:

$$X = \overline{A}\overline{B}\overline{C}\overline{D}\overline{E} + \overline{A}\overline{B}C\overline{D}\overline{E} + \overline{A}\overline{B}CDE + \overline{A}\overline{B}\overline{C}D\overline{E} + \overline{A}\overline{B}\overline{C}DE + \overline{A}\overline{B}CDE + \overline{A}BC\overline{D}\overline{E} + \overline{A}BCDE + \overline{A}B\overline{C}D\overline{E} + \overline{A}B\overline{C}DE + \overline{A}BCDE + \overline{A}BCDE + \overline{A}BCDE$$



- Final Simplified Expression is,

$$X + \overline{A}\overline{D}\overline{E} + \overline{B}\overline{C}\overline{D} + BCE + ACDE$$

