



Sequential Logic

Rab Nawaz Khan Jadoon

Lecturer

COMSATS Lahore

Pakistan

Department of Computer Science


DCS

COMSATS Institute of
Information Technology

Digital Logic and Computer Design

Sequential Logic

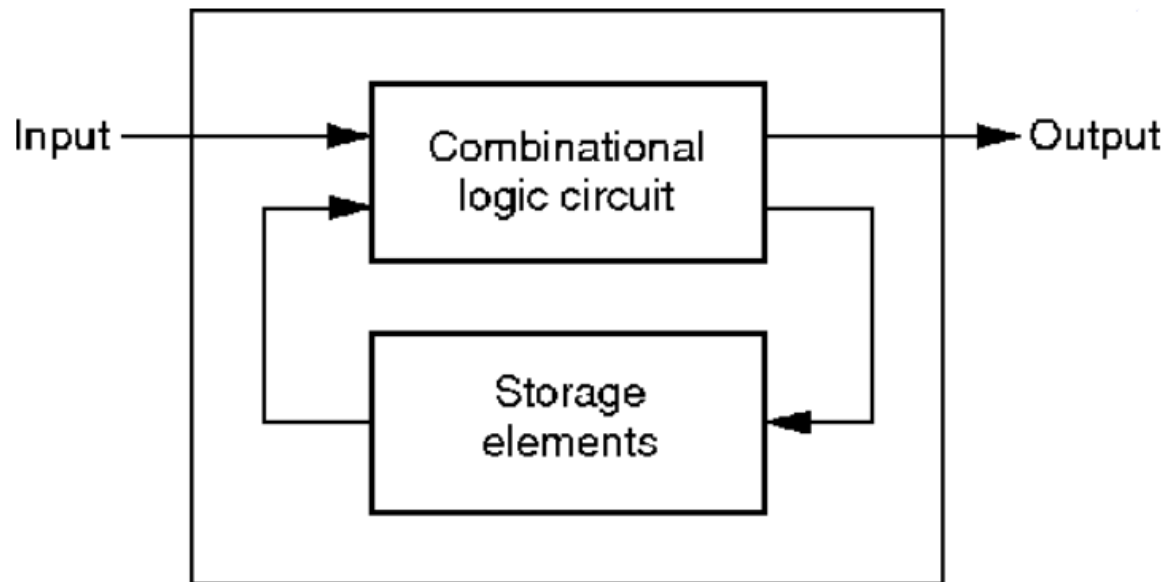- Combinational circuits with memory elements called **sequential logic**.
- Block diagram of the sequential logic is,



Sequential Logic

- **Sequential circuit** consists of combinational logic circuit to which memory elements are connected to form a feedback path.
- **Memory elements** are devices capable of storing binary information within them.
- The binary information stored in the memory elements at any given time defines the **state** of the sequential circuits.
- **For example**, ALU Operation, MUX and DeMUX, The Counter Circuits etc


Latches and Flip Flops

- **A latch** is a temporary storage device that has two stable states.
- Its output can be changed by applying appropriate inputs.
- **A latch** normally has two inputs, and two outputs Q and Q' .
- The **Latch** is said to be in Logic High when,
 - $Q=1$ and $Q'=0$
 - And vice versa.

- A **Latch is memory element** which is able to retain the information stored in it.
- Flip flop circuit can be constructed from **two NAND or NOR Gates**.
- The cross coupled connection constitute a feedback.
- Such type of circuits are also called ***direct coupled RS flip flop or SR latch***.

Basic Flip Flop Circuit

 
- The figure describes the circuit as follow,



Basic Flip Flop Circuit

- To analyze the operation of the circuits on previous slide,
 - We know that the output of the NOR gate is 0 if any input is one, and vice versa.
 - Starting for the draw run take all the possibilities,
 - Set=1 and Reset=0 then $Q=1$ and $Q'=0$
 - Set=0 and Reset=0 then $Q=1$ and $Q'=0$ Memory
 - Set=0 and Reset=1 then $Q=0$ and $Q'=1$
 - Set=0 and Reset=0 then $Q=0$ and $Q'=1$ Memory
 - Set=1 and Reset=1 then $Q=0$ and $Q'=0$
(Indeterminate state)

Flip Flop with NAND Gates

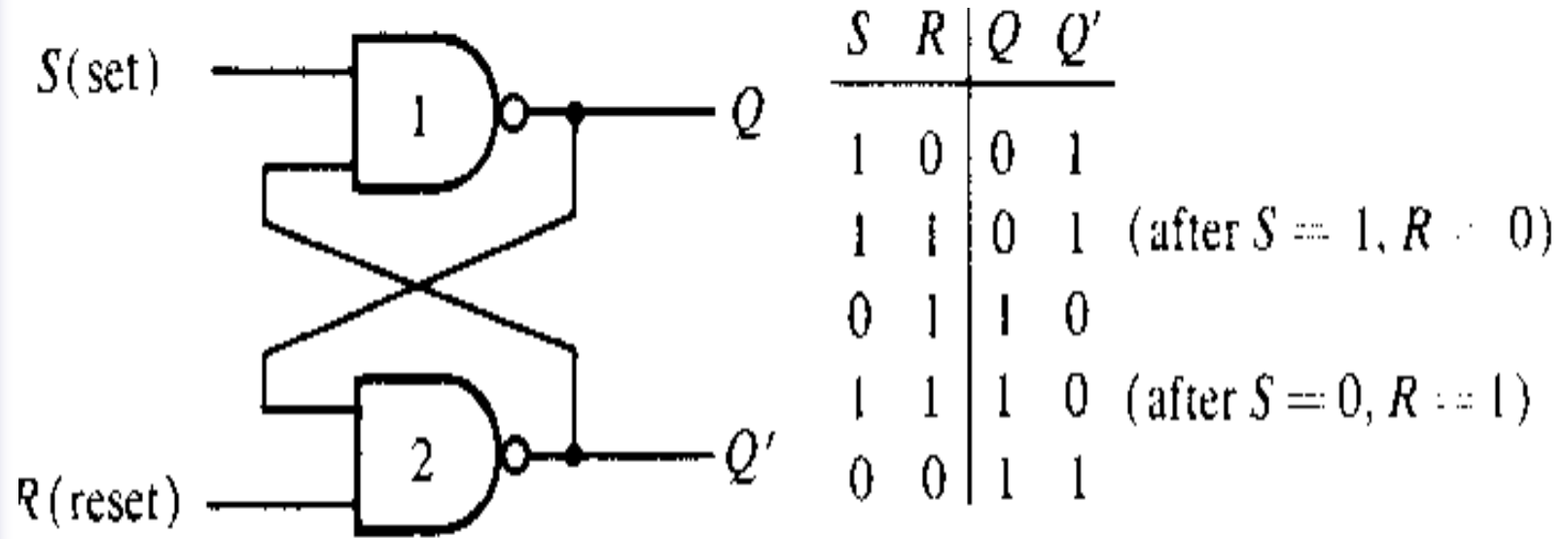

(a) Logic diagram


(b) Truth table

For S=1, R=1, Q=0, Q'=1 after S=1, R=0 → Memory
 For S=1, R=1, Q=1, Q'=0 after S=0, R=1 → Memory


RS-Flip Flop

- The operation of the basic flip flop can be modified by providing an additional control input that determines when the state of the circuit is to be changed.
- An **RS flip flop** with a clock pulse(CP) is shown.
- It consists of basic flip flop circuit and two additional NAND gates.
- CP acts as an enable signal input.

RS-Flip Flop

 


Q	S	R	Q(t+1)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	Invalid
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	invalid

 

$$Q(t + 1) = S + R'Q$$

$$SR = 0$$

(c) Characteristic equation

 


- One way to eliminate the undesirable condition of the indeterminate state in the RS flip flop is to ensure that inputs S and R are never Equal to 1 at the same time.
- It has only two inputs D and CP.
- The D input directly goes to the S input and its complement is applied to R input.
- As long as the pulse input is at 0, the outputs of the gates 3 and 4 are at the one level and the circuit cannot change state regardless of the value of D.


D-Flip Flop

- If $D=1$,
 - Q output goes to 1, placing the circuit in the set state.
- If $D=0$,
 - Output Q goes to 0, and circuit switches to the clear state.

D-Flip Flop

 


(a) Logic diagram with NAND gates

 

(b) Graphical symbol

Q	D	Q(t+1)
0	0	0
0	1	1
1	0	0
1	1	1

(c) Transition table

 


(c) Characteristic equation

- A **JK flip flop** is a refinement of the RS flip flop to overcome the indeterminate states.
- Input J and K behave like inputs S and R to Set and Clear the flip flop.
- J for Set and K for Reset.
- A **JK flip flop** is constructed with two cross coupled NOR gates and two AND gates.
- Output Q is ANDed with K and CP inputs
- so that the FF is cleared during a CP only if Q was previously 1.

JK-Flip Flop

 - Output Q' is ANDed with J and CP inputs so that FF is set with a CP only when Q' was previously 1.



(a) Logic diagram

Q	J	K	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Characteristic Table

JK-Flip Flop

		<i>JK</i>		<i>J</i>	
		00	01	11	10
<i>Q</i>	0			1	1
	1	1			1

K


$$Q(t + 1) = JQ' + K'Q$$

(c) Characteristic equation


T-Flip Flop

- It's a single input version of **JK flip flop**.
- The destination T comes from the ability of the FF to **"toggle"**, or complement its state.
- The **characteristic table and equation** show that when $T=0$, $Q(t+1)=Q$, that is, the next state is the same as the present state and no change occurs.
- When $T=1$, then $Q(t+1)=Q'$ and the state of the FF is complemented.

T-Flip Flop

 

(a) Logic diagram

 

(b) Graphical symbol

Q	T	Q(t+1)
0	0	0
0	1	1
1	0	1
1	1	0

(c) Transition table

		T	
		0	1
Q	0		1
	1	1	

$$Q(t+1) = TQ' + T'Q$$

(c) Characteristic equation

Master Slave Flip Flop

- A **Master Slave** FF is constructed from two separate FF.
- One circuit serves as a master and other as a slave, and the overall circuit is called to as a **Master Slave Flip Flop**.

